

Final Project

Finite State Machine

Cow Drinks

Emma Burkett

07/23/2024

Description of the Project:

This project has five states that indicate when a 'cow' should drink water and expel the water. The drinking is controlled by the potentiometer and the current state is indicated by the offboard red, yellow, and green LEDs. The state is also indicated by the seven-segment display. The analog input is displayed by the on-board LEDs for testing as sometimes the potentiometer is a little finicky.

First Peer Review:

Jared suggested taking our original reminder to drink water for a human and turn it into a cow. The project was much more interesting this way, so we changed it.

Michael suggested that we make our timer module accommodate all our timers into one always block. This added an interesting addition to our finite state machine.

Second Peer Review:

We didn't remember to do an official second peer review, but we did have quite a few peers look over our project, like Val and Jerad. And they were very positive and supportive.

Conclusion Statement:

The finite state machine, the seven segment display, and the off-board LEDs had 100% functionality. Incorporating Brother Jack's modified ADC code proved difficult. We got it to run but it would occasionally have errors due to how our timers were set up. The seven-segment display would sometimes display values that we did not write. We also should have included a default value for our seven-segment display, but we ran out of time.

Other than that one error our code functioned as expected so in total we had about 99% functionality. Our Video demonstration does not include the potentiometer in it because we ran out of time, and we had already demonstrated it to Brother Jack.

Because our output logic relies on the next state instead of the current state the finite state machine is Mealy than Moore because the outputs do not wait for the clock cycle. This was an error born from misunderstanding lab 7 and the fact that the pulses happened a clock cycle too late, and the states would change unexpectedly on us. Brother Jack told us we could simulate it and identify the error and that would probably fix the seven-segment display but unfortunately due to time constraints we never got to it.

Please see the PDF for Finite State Machine details.

Code for test bench:

```
module state_machine_top_tb(


);
// This is a basic testbench for the finite state machine
reg clk;
reg btnC;
wire [6:0] JC;
wire [7:0] JB;

// Instance of the state machine.
state_machine_top state_inst(.clk(clk), .btnC(btnC),
                             .JC(JC), .JB(JB));


// Run the clock at 10MHz
always #5 clk = !clk;

initial
    begin
        // Instantiate values like clk and reset(BTNC)
        clk = 1;
        btnC = 0;
        #20 btnC = 1;
        #20 btnC = 0;
        #1000 $finish;
    end
endmodule
```

Test Bench images for finite state machine only!:

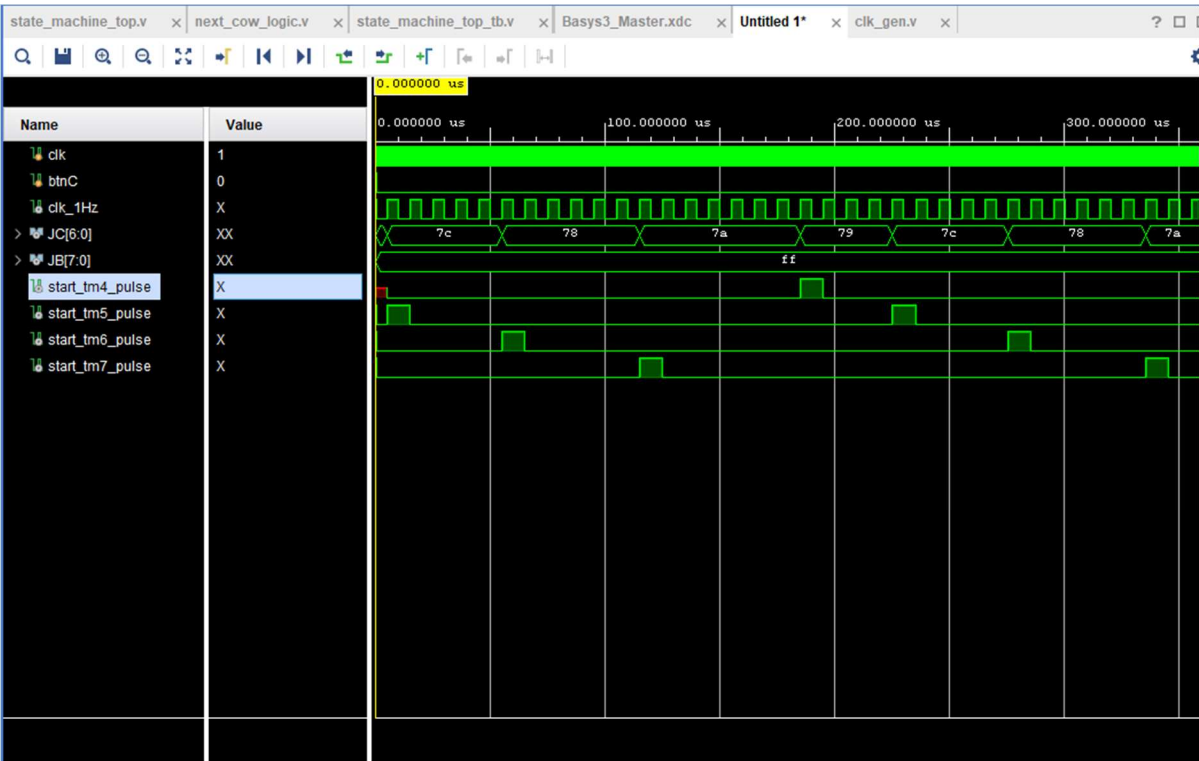


 Simulation 1: Finite state Machine Test Bench




Implementation 1: Finite State Machine Only

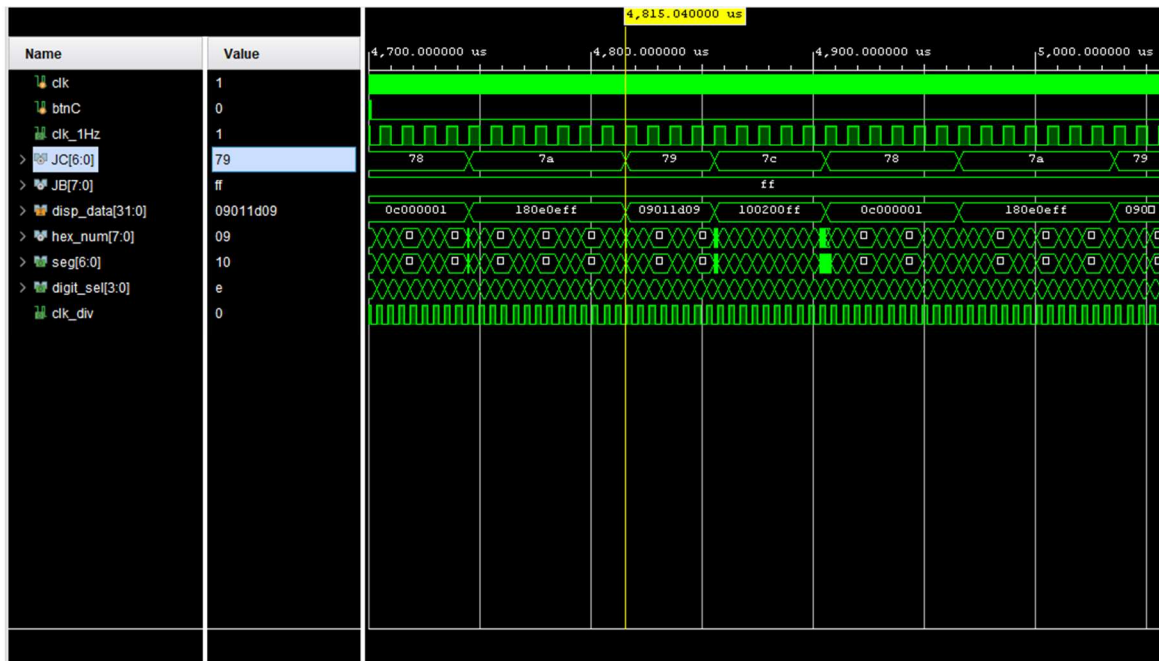
Test bench images for finite state Machine and seven seg display:




Simulation 2: After instantiating the seven segment display code we ran the same test bench again. It probably should not have worked because we didn't pass in an, seg, and dp into our state machine instantiation but it did.

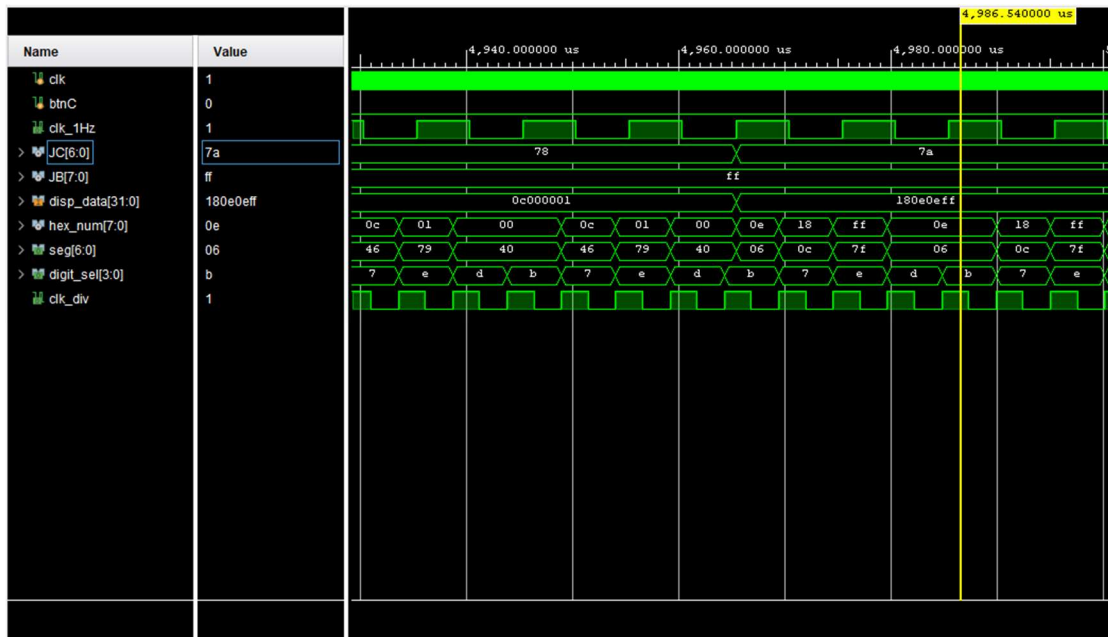

Simulation 2b: Zoomed in to see the an[3:0] value changing and the seg[6:0] value.

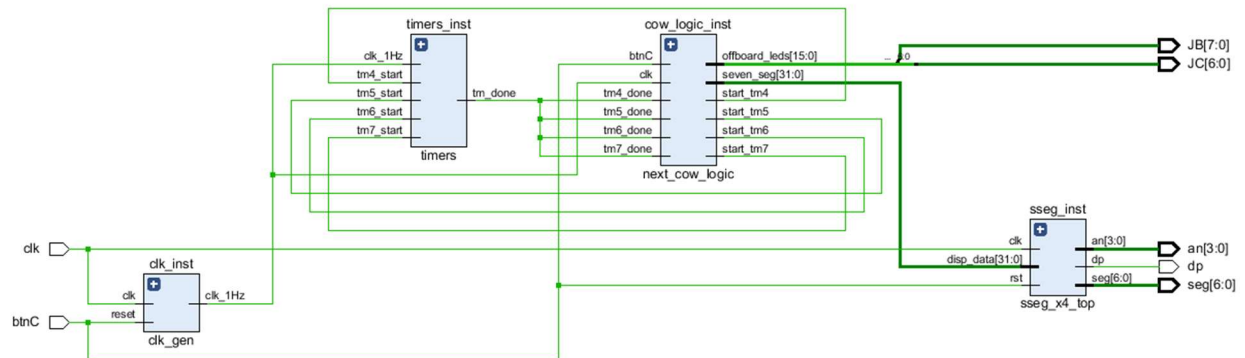

 Schematic 1: This schematic is cool because it is so visible it is only the state machine and the segment display.




Implementation 2: Finite state machine and seven segment display

Additional Project Description and Video:


Here is our video demonstration on YouTube. It does not include the potentiometer; however we did demonstrate that functionality to Brother Jack on Monday or Friday. It does include the 7-segment display and the off board LEDs. The off board LEDs form the word cow, and they have three LEDs that turn on corresponding to what state you are in. You can refer to the PDF submitted with this document that outlines how long each state lasts and which red, yellow, or green LED lights up. The only state not demonstrated here is the 'cow dead' state as the cow dead state needs the potentiometer to have functionality.

<https://youtu.be/75OV4b0kyMk>


 
Images for the whole project: Note no simulation for the ADC data due to time constraints.



Implementation 3: Finite State Machine, Seven Seg Display, and Potentiometer.

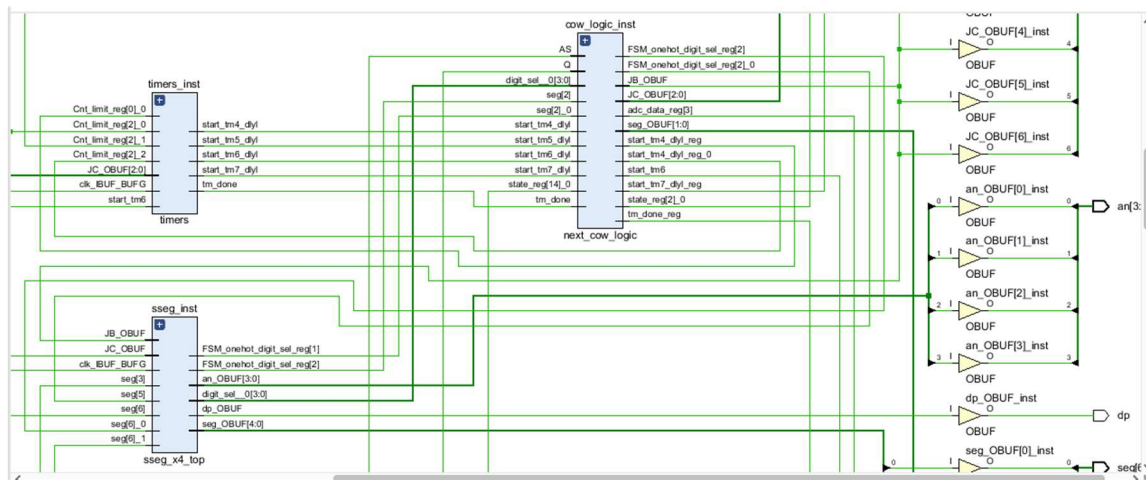

Schematic 2: Finite State Machine, Seven Seg Display, and Potentiometer

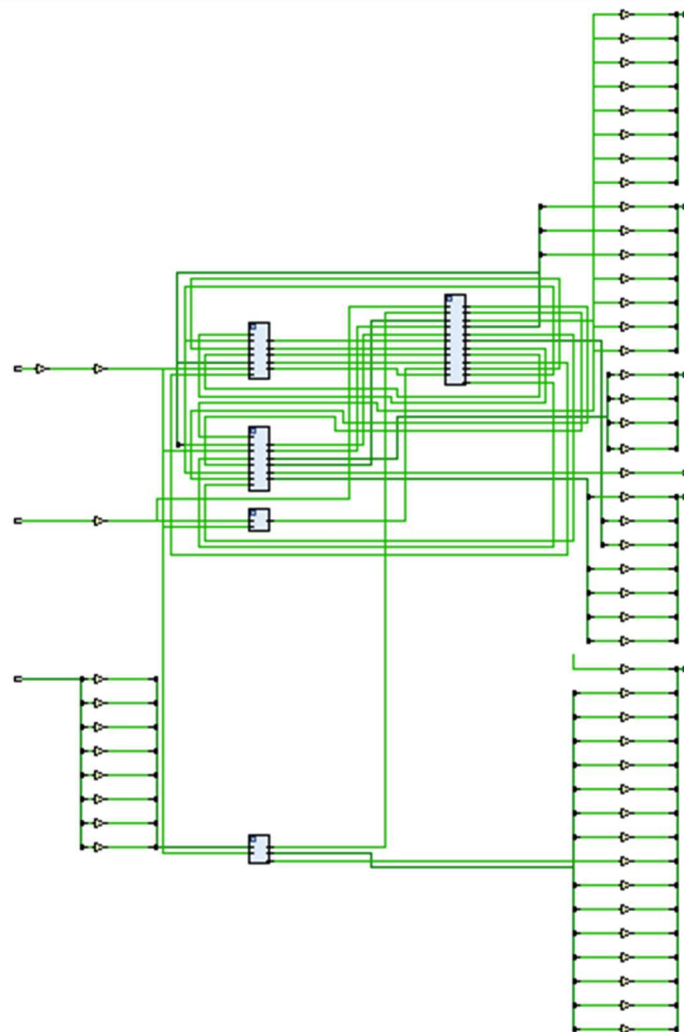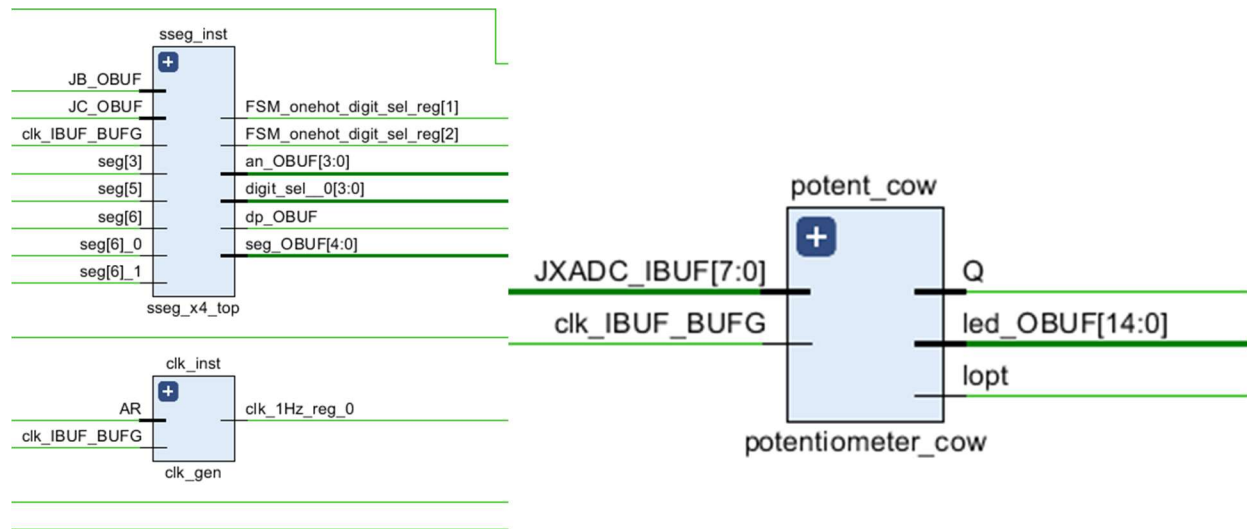

Schematic 2b: Closer Images and Overview

Top Module

```
module state_machine_top(
    input clk, btnC,
    input  [7:0] JXADC,
    output [6:0] JC,
    output [7:0] JB,
    output [15:0] led,
    output [6:0] seg,
    output [3:0] an,
    output      dp
);
    wire [11:0] adc_data;
    wire [14:0] offboard_leds;
    assign JB = offboard_leds[14:7];
    assign JC = offboard_leds[6:0];
    wire [31:0] seven_seg;

    clk_gen clk_inst(.clk(clk), .reset(btnC),
        .clk_1Hz(clk_1Hz));

    next_cow_logic cow_logic_inst(
        .tm4_done(tm_done),
        .tm5_done(tm_done),
        .tm6_done(tm_done),
        .tm7_done(tm_done),
        .clk(clk_1Hz),
        .btnC(btnC),
        .start_tm5(start_tm5),
```

```
.start_tm4(start_tm4),  
.start_tm6(start_tm6),  
.start_tm7(start_tm7),  
.next_state(next_state),  
.seven_seg(seven_seg),  
.offboard_led(offboard_leds),  
.water_content(adc_data)  
);
```

```
timers timers_inst(  
    .tm4_start(start_tm4),  
    .tm5_start(start_tm5),  
    .tm6_start(start_tm6),  
    .tm7_start(start_tm7),  
    .clk_1Hz(clk),  
    .tm_done(tm_done)  
);
```

```
potentiometer_cow potent_cow(  
    .clk(clk),  
    .JXADC(JXADC),  
    .led(led),  
    .adc_data(adc_data)  
);
```

```
sseg_x4_top sseg_inst(  
    .seg(seg),
```

```
.an(an),  
.dp(dp),  
.clk(clk),  
.rst(btnC),  
.disp_data(seven_seg)  
);
```

```
endmodule
```

1 Hz Clock:

```
module clk_gen(  
    input clk, reset,  
    output reg clk_1Hz  
);  
    //reg [15:0] Q;  
    reg [26:0] Q;  
    always @(posedge clk, posedge reset)  
        if (reset)  
            begin  
                Q <= 0;  
                clk_1Hz <= 0;  
            end  
        else if (Q < 500000000)  
            Q <= Q +1;  
        else  
            begin  
                Q <= 0;  
                clk_1Hz <= !clk_1Hz;  
            end  
endmodule
```

Next State Logic:

```
module next_cow_logic(
    input tm6_done, tm7_done, tm5_done, tm4_done, clk, btnC,
    [11:0] water_content,
    output reg start_tm5, start_tm4, start_tm7, start_tm6,
    output reg [14:0] next_state,
    output reg [31:0] seven_seg,
    output reg [14:0] offboard_led
);

    wire [14:0] cow_drinks;
    wire [14:0] cow_happy;
    wire [14:0] cow_potty;
    wire [14:0] cow_thirst;
    wire [14:0] cow_dead;

    assign cow_drinks [14:0] = 15'b1111111111111100;
    assign cow_happy [14:0] = 15'b1111111111111000;
    assign cow_potty [14:0] = 15'b1111111111111010;
    assign cow_thirst [14:0] = 15'b1111111111111001;
    assign cow_dead [14:0] = 15'b0000000000000000;

    reg [14:0] state;

    //Flip flops for state
    always @(posedge clk, posedge btnC)
        if (btnC)
            state <= cow_thirst;
        else
```

```

        state <= next_state;

always @ *
    case(state)
        cow_drinks:
            if(water_content[3] == 1'b1 && tm5_done)
                next_state = cow_happy;
            else if (water_content[3] == 1'b0 && tm5_done)
                next_state = cow_dead;
            else
                next_state = cow_drinks;
        cow_happy:
            if (tm6_done)
                next_state = cow_potty;
            else
                next_state = cow_happy;
        cow_potty:
            if (water_content[3] == 0'b0 && tm7_done)
                next_state = cow_thirst;
            else if (water_content[3] == 1'b1 && tm7_done)
                next_state = cow_dead;
            else
                next_state = cow_potty;
        cow_thirst:
            if (tm4_done)
                next_state = cow_drinks;
            else

```



```

        next_state = cow_thirst;
cow_dead:
    next_state = cow_dead;
default:
    next_state <= cow_thirst;
endcase
// Output logic
always @(next_state)
    case(next_state)
        cow_drinks: //0h20
            begin
                start_tm4 = 0;
                start_tm5 = 1;
                start_tm6 = 0;
                start_tm7 = 0;
                offboard_led = cow_drinks;
                seven_seg = 32'h100200ff;
            end
        cow_happy: //c001
            begin
                start_tm4 = 0;
                start_tm5 = 0;
                start_tm6 = 1;
                start_tm7 = 0;
                offboard_led = cow_happy;
                seven_seg = 32'h0c000001;
            end
    endcase
end

```

```

cow_potty: //pee
    begin
        start_tm4 = 0;
        start_tm5 = 0;
        start_tm6 = 0;
        start_tm7 = 1;
        offboard_led = cow_potty;
        seven_seg = 32'h180e0eff;
    end
cow_thirst: //glug
    begin
        start_tm4 = 1;
        start_tm5 = 0;
        start_tm6 = 0;
        start_tm7 = 0;
        offboard_led = cow_thirst;
        seven_seg = 32'h09011d09;
    end
cow_dead: //beef
    begin
        start_tm4 = 0;
        start_tm5 = 0;
        start_tm6 = 0;
        start_tm7 = 0;
        offboard_led = cow_dead;
        seven_seg = 32'h0b0e0e0f;
    end

```

```
default:
    begin //potty
        start_tm4 = 0;
        start_tm5 = 0;
        start_tm6 = 0;
        start_tm7 = 1;
        offboard_led = cow_potty;
        seven_seg = 32'h190e0eff;
    end
endcase

endmodule
```

// Timers for 4, 5, 6, & 7 seconds

```
module timers(  
    input tm4_start, tm5_start, tm6_start, tm7_start, clk_1Hz,  
    output reg tm_done  
);  
  
    wire start_tm4_pulse;  
    wire start_tm5_pulse;  
    wire start_tm6_pulse;  
    wire start_tm7_pulse;  
  
    reg [2:0] Cnt;  
    reg [2:0] Cnt_limit;  
    reg start_tm4_dly1;  
    reg start_tm5_dly1;  
    reg start_tm6_dly1;  
    reg start_tm7_dly1;  
  
    always @ (posedge clk_1Hz)  
        begin  
            start_tm4_dly1 <= tm4_start;  
            start_tm5_dly1 <= tm5_start;  
            start_tm6_dly1 <= tm6_start;  
            start_tm7_dly1 <= tm7_start;  
        end  
  
    assign start_tm4_pulse = tm4_start && !start_tm4_dly1;
```

```

assign start_tm5_pulse = tm5_start && !start_tm5_dly1;
assign start_tm6_pulse = tm6_start && !start_tm6_dly1;
assign start_tm7_pulse = tm7_start && !start_tm7_dly1;
// Integrated clock signals!
always @ (posedge clk_1Hz)
    if (start_tm4_pulse)
        begin
            Cnt <= 0;
            tm_done <= 0;
            Cnt_limit <= 2;
        end
    else if (start_tm5_pulse)
        begin
            Cnt <= 0;
            tm_done <= 0;
            Cnt_limit <= 3;
        end
    else if (start_tm6_pulse)
        begin
            Cnt <= 0;
            tm_done <= 0;
            Cnt_limit <= 4;
        end
    else if (start_tm7_pulse)
        begin
            Cnt <= 0;
            tm_done <= 0;

```

```
        Cnt_limit <= 5;
    end
    else if (Cnt < Cnt_limit)
        Cnt <= Cnt +1;
    else
        tm_done <= 1;
    endmodule
```

```
// Brother Jacks modified code - we remove the seven segment  
display and output adc_data
```

```
module potentiometer_cow(  
    input clk,  
    input [7:0] JXADC,  
    output reg [15:0] led,  
    output reg [11:0] adc_data  
);
```

```
    wire [15:0] data_out; //Dynamic Reconfiguration Port (DRC)  
data output
```

```
    wire [15:0] data_in; // DRC data input
```

```
    wire [15:0] aux_channel_n, aux_channel_p; // Analog  
differential inputs
```

```
    wire [6:0] DRP_address_in; //
```

```
    wire eoc_pulse; // use "End of Conversion" (EOC) to enable  
DRP
```

```
    wire dwe_in; // DRC write enable
```

```
assign DRP_address_in = 7'h16;
```

```
// Analog inputs
```

```
assign aux_channel_p = {JXADC[3], JXADC[1], 6'bzz_zzzz,  
JXADC[2], JXADC[0], 6'bzz_zzzz};
```

```
assign aux_channel_n = {JXADC[7], JXADC[5], 6'bzz_zzzz,  
JXADC[6], JXADC[4], 6'bzz_zzzz};
```

```

assign dwe_in = 1'b0;

/* INIT_40 description
15 14 13 12 11 10 9 8 7 6 5
4 3 2 1 0
CAVG, 0, AVG1, AVG0, MUX, Bip/Uni', Event/Cont', ACQ, 0, 0, 0,
CH4, CH3, CH2, CH1, CH0
CAVG = 1 to disable Calibration Averaging
AVG1, AVG0: 00 No Sample Averaging, 01 Average 16, 10 Average
64, 11 Average 256
MUX = 1 to enable external Multiplexer Mode
ACQ = 1 to increase settling time to 6 clock cycles (single chan
mode)
CH4 CH3 CH2 CH1 CH0
00000 On-Chip temp
00001 VCCINT
00010 VCCAUX
00011 VP, VN
00100 VREFP (1.25V)
00101 VREFN (0V)
00110 VCCBRAM
01101 VCCPINT
01110 VCCPAUX
01111 VCCO_DDR
1XXXX Select Auxiliary Input Channel XXXX (0-15)*/
/* INIT_41 description
15 14 13 12 11 10 9 8 7 6 5
4 3 2 1 0

```



```

SEQ3, SEQ2, SEQ1, SEQ0, ALM6, ALM5, ALM4, ALM3, CAL3, CAL2,
CAL1, CAL0, ALM2, ALM1, ALM0 OT

SEQ3 SEQ2 SEQ1 SEQ0

0000 Default sequencer (monitors default voltages)
0001 Single pass sequence
0010 Continuous Sequence mode
0011 Single channel mode (Sequencer off)
01xx Simultaneous sampling mode
10xx Independent ADC mode
11xx Default mode

CAL3 = 1 Enables Supply sensor offset and gain correction
CAL2 = 1 Enables Supply sensor offset correction
CAL1 = 1 Enables ADC offset and gain correction
CAL0 = 1 Enables ADC offset correction
ALMx = 1 to disable respective alarm
OT = 1 to disable Over temperature signal */

/* INIT_42 description
 15   14   13   12   11   10    9    8   7   6   5    4   3   2   1
0
CD7, CD6, CD5, CD4, CD3, CD2, CD1, CD0, 0, 0, PD1, PD0, 0, 0, 0,
0

CD7-CD0 Sets the DCLK division (minimum is 2, maximum is 255)
PD1 PD0

00 = ALL ADC Blocks powered up
10 = ADC B powered down
11 = XADC Blocks powered down */

//xadc instantiation connect the eoc_out .den_in to get
continuous conversion

```

```

XADC #(
// Initializing the XADC Control Registers

.INIT_40(16'h8016),//For Aux6 continuous sampling and no
averaging: 16'h8016

.INIT_41(16'h3fff),//For Single channel, all alarms off, all
calibration off: 16'h3fff

.INIT_42(16'h0400),// Set DCLK divider to 4, ADC = 1Msps, DCLK =
100MHz

// not using the following registers

.INIT_48(16'h0000),// not using sequencer

.INIT_49(16'h0000),// not using sequencer

.INIT_4A(16'h0000),// not using averaging

.INIT_4B(16'h0000),// No averaging on external channels

.INIT_4C(16'h0000),// Sequencer Bipolar selection

.INIT_4D(16'h0000),// Sequencer Bipolar selection

.INIT_4E(16'h0000),// Sequencer Acq time selection

.INIT_4F(16'h0000),// Sequencer Acq time selection

.INIT_50(16'hb5ed),// Temp upper alarm trigger 85°C

.INIT_51(16'h5999),// Vccint upper alarm limit 1.05V

.INIT_52(16'hA147),// Vccaux upper alarm limit 1.89V

.INIT_53(16'h0000),// OT upper alarm limit 125°C using automatic
shutdown

.INIT_54(16'ha93a),// Temp lower alarm reset 60°C

.INIT_55(16'h5111),// Vccint lower alarm limit 0.95V

.INIT_56(16'h91Eb),// Vccaux lower alarm limit 1.71V

.INIT_57(16'hae4e),// OT lower alarm reset 70°C

.INIT_58(16'h5999),// VCCBRAM upper alarm limit 1.05V

.INIT_5C(16'h5111)// VCCBRAM lower alarm limit 0.95V

//.SIM_MONITOR_FILE("sensor_input.txt")

```

```

// Analog Stimulus file. Analog input values for simulation
)

XADC_INST ( // Connect up instance IO. See UG480 for port
descriptions

.CONVST(GND_BIT), // not used

.CONVSTCLK(GND_BIT), // not used

.DADDR(DRP_address_in),

.DCLK(clk),

.DEN(eoc_pulse),

.DI(data_in),

.DWE(dwe_in),

.RESET(), // not used

.VAUXN(aux_channel_n[15:0]),

.VAUXP(aux_channel_p[15:0]),

.ALM(),

.BUSY(),

.CHANNEL(),

.DO(data_out),

.DRDY(),

.EOC(eoc_pulse),

.EOS(),

.JTAGBUSY(), // not used

.JTAGLOCKED(), // not used

.JTAGMODIFIED(), // not used

.OT(),

.MUXADDR(), // not used

.VP(VP_IN),

.VN(VN_IN)

```

```
);
```

```
always @ (posedge clk)
    if (eoc_pulse)
        begin
            adc_data <= data_out >> 4;
        end
```

```
//led thermometer dmm
```

```
always @(adc_data)
begin
    case (adc_data[11:8])
        1: led <= 16'b0000000000000011;
        2: led <= 16'b0000000000000111;
        3: led <= 16'b0000000000001111;
        4: led <= 16'b0000000000011111;
        5: led <= 16'b0000000000111111;
        6: led <= 16'b0000000001111111;
        7: led <= 16'b0000000011111111;
        8: led <= 16'b0000000111111111;
        9: led <= 16'b0000001111111111;
        10: led <= 16'b0000011111111111;
        11: led <= 16'b0000111111111111;
        12: led <= 16'b0001111111111111;
        13: led <= 16'b0011111111111111;
        14: led <= 16'b0111111111111111;
        15: led <= 16'b1111111111111111;
```

```
        default: led <= 16'b0000000000000001;  
    endcase  
end  
endmodule
```

```

module sseg_x4_top(
    output [6:0] seg,
    output [3:0] an,
    output      dp,
    input       clk,
    input       rst,
    input  [31:0] disp_data
);
    wire clkd;
    wire [7:0] hex_num;

    /* Divides the clock */
    clk_gen_SEG clk_gen_SEG_inst(.clk_div(clkd), .clk(clk),
    .rst(btnC));

    /* Selects the digit */
    digit_selector digit_selector(.digit_sel(an), .clk(clkd),
    .rst(btnC));

    /* Decided which switches to listen to */
    hex_num_gen hex_num_gen(.hex_num(hex_num), .digit_sel(an),
    .sw(disp_data));

    /* The display */
    sseg_display sseg(.seg(seg), .dp(), .sw(hex_num));

    assign dp = (an == 4'b0111)?1'b0:1'b1;

```

endmodule

```

module clk_gen_SEG(
    output clk_div,
    input  clk,
    input  rst
);
    reg [25:0] cntr;          // Holds the 26-bit count
    assign clk_div = cntr[18]; // bit 18 is 190 Hz, bit 17 is
380 Hz

    /* Implements the 26-bit counter */
    always @ (posedge clk, posedge rst)
        begin
            if (rst)
                cntr <= 26'b0;          // Resets the counter
            else if (clk)
                cntr <= cntr + 1; // Increment the counter each
clock tick
        end

endmodule

```



```

/* Determines which digit is lit up */
always @ (posedge clk, posedge rst)
begin
    if (rst)
        digit_sel <= 4'b1110; // Resets to the least
significant digit
    else
        case (digit_sel)
            4'b1110:
                digit_sel <= 4'b1101;
            4'b1101:
                digit_sel <= 4'b1011;
            4'b1011:
                digit_sel <= 4'b0111;
            4'b0111:
                digit_sel <= 4'b1110;
            default:
                digit_sel <= 4'b1110;
        endcase
    end
endmodule

```

```
/* Generates the number that syncs the switches with the correct
digit */
```

```
module hex_num_gen(
```

```
    output reg [7:0] hex_num,
```

```
    input  [3:0] digit_sel,
```

```
    input [31:0] sw
```

```
);
```

```
/* Generates the number that syncs the switches with the
correct digit */
```

```
    always @ (*)
```

```
        begin
```

```
            case (digit_sel)
```

```
                4'b1110: hex_num = sw[7:0];    // Sets the first
digit
```

```
                4'b1101: hex_num = sw[15:8];    // Sets the
second digit
```

```
                4'b1011: hex_num = sw[23:16];    // Sets the
third digit
```

```
                4'b0111: hex_num = sw[31:24];    // Sets the
fourth digit
```

```
                default: hex_num = 8'b00000001;    // Turns it
off
```

```
            endcase
```

```
        end
```

```
endmodule
```

```

module sseg_display(
    output reg [6:0] seg,
    output dp,
    input [7:0] sw
);
assign dp = 1'b1;      // Force the decimal point off

/* Change the number on the display each time a different
   sequence of switches are flipped */
always @ (sw)
    begin
        if(sw == 8'h00)      seg = 7'b1000000; //0
        else if (sw == 8'h01) seg = 7'b1111001; //1
        else if (sw == 8'h02) seg = 7'b0100100; //2
        else if (sw == 8'h03) seg = 7'b0110000; //3
        else if (sw == 8'h04) seg = 7'b0011001; //4
        else if (sw == 8'h05) seg = 7'b0010010; //5
        else if (sw == 8'h06) seg = 7'b0000010; //6
        else if (sw == 8'h07) seg = 7'b1111000; //7
        else if (sw == 8'h08) seg = 7'b0000000; //8
        else if (sw == 8'h09) seg = 7'b0010000; //9
        else if (sw == 8'h0a) seg = 7'b0001000; //A
        else if (sw == 8'h0b) seg = 7'b0000011; //b
        else if (sw == 8'h0c) seg = 7'b1000110; //C
        else if (sw == 8'h0d) seg = 7'b0100001; //d
        else if (sw == 8'h0e) seg = 7'b0000110; //E
        else if (sw == 8'h0f) seg = 7'b0001110; //F
    end

```

```

else if (sw == 8'h10) seg = 7'b0001001; //H
else if (sw == 8'h18) seg = 7'b0001100; //P
else if (sw == 8'h1d) seg = 7'b1000001; //U
else if (sw == 8'hff) seg = 7'b1111111; // blank
else if (sw == 8'hf0) seg = 7'b1001100; // first
part m
else if (sw == 8'hf1) seg = 7'b1011000; // last half
else seg = 7'b1111111;

//          //H20 //mad // f0f10a0d
//          else if (sw == 8'h10) seg = 7'b0001001; //H
//          else if (sw == 4'h2) seg = 7'b0100100; //2
//          if (sw == 4'h0) seg = 7'b1000000; //0

//          //CO01
//          else if (sw == 4'hc) seg = 7'b1000110; //C
//          if (sw == 4'h0) seg = 7'b1000000; //0
//          if (sw == 4'h0) seg = 7'b1000000; //0
//          else if (sw == 4'h1) seg = 7'b1111001; //1

//          //PEE
//          else if (sw == 8'h18) seg = 7'b0001100; //P 190e0e
//          else if (sw == 4'he) seg = 7'b0000110; //E
//          else if (sw == 4'he) seg = 7'b0000110; //E

//          //bEEF
//          else if (sw == 4'hb) seg = 7'b0000011; //b
//          else if (sw == 4'he) seg = 7'b0000110; //E

```

```

//          else if (sw == 4'he) seg = 7'b00001110; //E
//          else if (sw == 4'hf) seg = 7'b00011110; //F //
0b0e0e0f

//          //91U9 glug
//          else if (sw == 8'h09) seg = 7'b0010000; //9
//          else if (sw == 8'h01) seg = 7'b1111001; //1
//          else if (sw == 8'h1d) seg = 7'b1000001; //U
//          else if (sw == 8'h09) seg = 7'b0010000; //9

//          //dEAd
//          else if (sw == 8'h0d) seg = 7'b0100001; //d
//          else if (sw == 8'h0e) seg = 7'b00001110; //E
//          else if (sw == 8'h0a) seg = 7'b0001000; //A
//          else if (sw == 8'h0d) seg = 7'b0100001; //d

    end

endmodule

```

Description of the Project:

This project has five states that indicate when a 'cow' should drink water and expel the water. The drinking is controlled by the potentiometer and the current state is indicated by the offboard red, yellow, and green LEDs. The state is also indicated by the seven-segment display. The analog input is displayed by the on-board LEDs for testing as sometimes the potentiometer is a little finicky.

First Peer Review:

Jared suggested taking our original reminder to drink water for a human and turn it into a cow. The project was much more interesting this way, so we changed it.

Michael suggested that we make our timer module accommodate all our timers into one always block. This added an interesting addition to our finite state machine.

Second Peer Review:

We didn't remember to do an official second peer review, but we did have quite a few peers look over our project, like Val and Jerad. And they were very positive and supportive.

Conclusion Statement:

The finite state machine, the seven segment display, and the off-board LEDs had 100% functionality. Incorporating Brother Jack's modified ADC code proved difficult. We got it to run but it would occasionally have errors due to how our timers were set up. The seven-segment display would sometimes display values that we did not write. We also should have included a default value for our seven-segment display, but we ran out of time.

Other than that one error our code functioned as expected so in total we had about 99% functionality. Our Video demonstration does not include the potentiometer in it because we ran out of time and we had already demonstrated it to Brother Jack.

Because our output logic relies on the next state instead of the current state the finite state machine is Mealy than Moore because the outputs do not wait for the clock cycle. This was an error born from misunderstanding lab 7 and the fact that the pulses happened a clock cycle too late, and the states would change unexpectedly on us. Brother Jack told us we could simulate it and identify the error and that would probably fix the seven-segment display but unfortunately due to time constraints we never got to it.